LED lighthouse - SIMPLE complete circuit / revision 0.4

Regulated 5V / 5 white LEDs / motion in darkness / adjustable duration and speed / no TLC372

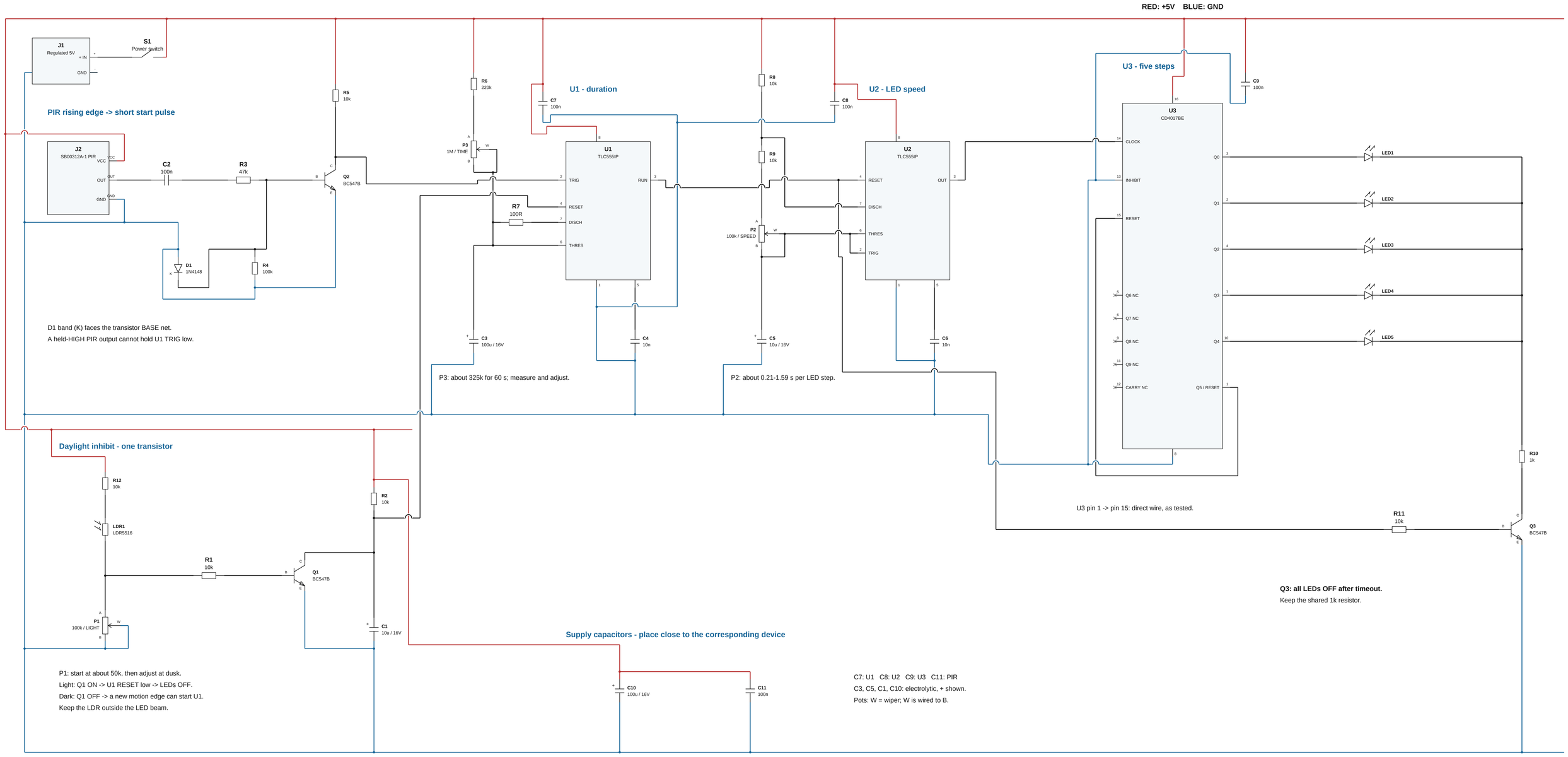

2026-10-30 / Complete combined circuit NOT hardware-tested. Follow the staged checks before permanent assembly.

Dot = connection. Bridge = crossing WITHOUT connection. All wires are drawn. Use printed pin numbers; symbol layout is functional.